

Building a Datapath, Review
What we're doing is figuring out what "functional units" we need to implement a representative subset of MIPS instructions.
Before the midterm, we talked about what's needed to store the program and step through it, and then what's needed for most of the instructions we want to implement.
Recall also that we have two kinds of functional units — CL blocks and state elements.

Slide 2

Slide 4



Building a Datapath — R-format Instructions
What we need to do: read contents of two registers, combine, store result in another register.
Datapath elements: register file, ALU.



Slide 5

Building a Datapath — Control-Flow Instructions

- What we need to do: For conditional branches, compute branch address from PC+4 and offset in instruction, subtract two registers and see if result is zero. For unconditional jumps, just replace PC with address from instruction.
- Datapath elements: register file, ALU, sign-extension unit, unit to do "left shift 2 bits"(really just routing), adder for PC.

(Why can't we just use the ALU to compute PC+4?)

• Connect them up as in igure 5.10.

Slide 6



Preview of Next Topic — Building a Simple "Control"

- Goal of next section finish designing a simple implementation of representative group of instructions.
- Simplify by requiring that all instructions must be completed in one clock cycle. Not optimally efficient, but simpler.

Slide 8

Basic idea will be to combine datapath elements sketched so far, figure out what "control signals" we need, then figure out how to generate them — using as input the current state of the machine and the instruction being executed.
 (E.g., the ALU needs an input telling it which operation to perform — "add" for loads/stores/branches, something based on instruction itself for R-format instructions, etc.)

